

LECTURE SERIES-03

DATE
25-04-20

B.Sc(H)-II
PAPER-IV

PHYSICS
ELECTRICITY

Dr. M. K. THAKUR
A. P. S. M. College, Barauni

Anderson's Bridge: This is one of the most accurate bridge for the measurement of self inductance in terms of a standard capacitance. In this bridge a variable non-inductive resistance is put in the detector arm, and the capacitor is connected across S and r. P, Q, R and S are the resistance, L is the self inductance of the coil and C is the standard capacitance of the capacitor. The complete circuit diagram of the bridge is shown in fig. (1)

Applying Kirchhoff's Law in the loop ABEA.

$$SI_1 - rI - \frac{I}{j\omega C} = 0$$

$$\text{or } SI_1 - I\left(r + \frac{1}{j\omega C}\right) = 0$$

$$\text{or } SI_1 = I\left(r + \frac{1}{j\omega C}\right)$$

$$\therefore I_1 = \frac{I\left(r + \frac{1}{j\omega C}\right)}{S} \quad \text{--- (1)}$$

From loop, AEDA,

$$\left(\frac{1}{j\omega C}\right)I - QI_2 = 0$$

$$\therefore I_2 = \left(\frac{1}{j\omega CQ}\right)I \quad \text{--- (2)}$$

From mesh BCDB,

$$R(I_1 + I) - (j\omega L + P)I_2 + rI = 0 \quad \text{--- (3)}$$

Putting the values of I_1 and I_2 in eqn (3), we have

$$R\left[I + \frac{\left(r + \frac{1}{j\omega C}\right)I}{S}\right] - (j\omega L + P)\left(\frac{1}{j\omega CQ}\right)I + rI = 0$$

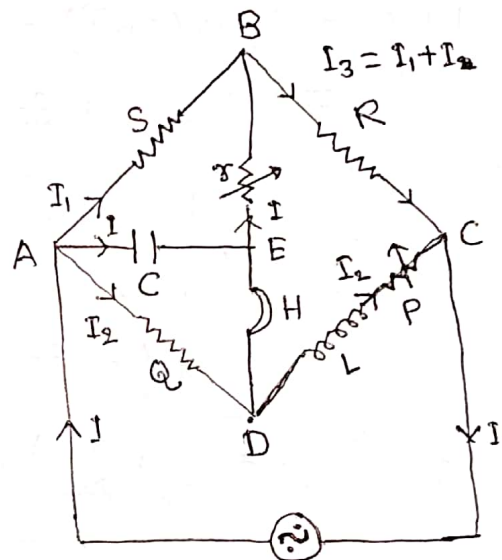


Fig. (1)

$$\text{or } \left[\frac{R}{S} r + R - \frac{L}{C\omega} + r + \frac{R}{S} \left(\frac{1}{j\omega C} \right) - \left(\frac{1}{j\omega C} \right) \frac{P}{Q} \right] I = 0 \quad \text{--- (4)}$$

[$\because I \neq 0$]

Equating real and imaginary parts of this equation, we have

$$\frac{R}{S} r + R - \frac{L}{C\omega} + r = 0$$

$$\therefore L = C\omega \left[r \left(1 + \frac{R}{S} \right) + R \right] \quad \text{--- (5)}$$

$$\text{and } \frac{1}{j\omega C} \cdot \frac{R}{S} = \frac{1}{j\omega C} \cdot \frac{P}{Q} = 0$$

$$\therefore \frac{P}{Q} = \frac{R}{S} \quad \text{--- (6)}$$

Hence, we can find L in terms of Q, R, S, r and Capacitance C using eqn (5). It is clear from eqn (5), that A.c balance is possible only when $L > CRQ$, otherwise r will be negligible. If $R = S$, then eqn (5) becomes

$$L = C\omega (R + 2r) \quad \text{--- (7)}$$

Hence C and r are adjusted for balance. For the bridge to be sensitive, $P = Q$

$$\therefore R = S = \frac{P}{2} \quad \text{and} \quad \frac{L}{C} = \frac{P^2}{2} \quad \text{--- (8)}$$

Vector Diagram: The vector diagram as shown in fig(2), Here OA represents the p.d between the terminals A and c or the potential vector for the applied source. If I_2 gives the current in mesh ADC , then $OC = I_2 Q$ and $CD = j\omega L I_2$ and $DA = P I_2$

Hence $DA \parallel OC$, and $CD \perp OC$ or DA

Since E and D are at the same potential, hence

$$V_{AE} = V_{AD} \quad (\text{In the circuit diagram})$$

Teacher's Signature: _____

$$\text{or } \left(\frac{1}{j\omega C}\right) I = Q I_2$$

Thus I is in quadrature with I_2 .
If $CB = rI$, then the vector OB is $S I_1$.

$$\text{The vector } OZ \text{ is } R I_2 = R(I_1 + I)$$

Thus, we can determine the direction of I_1 and I_2 from the diagram

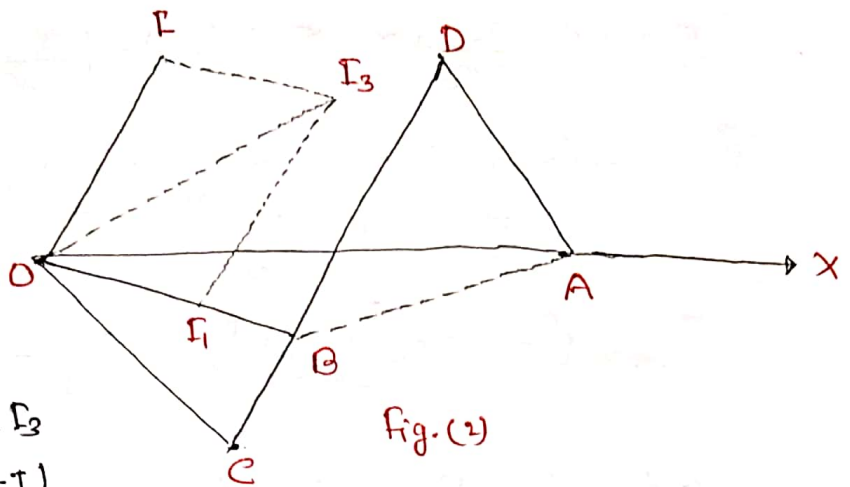


Fig. (2)

